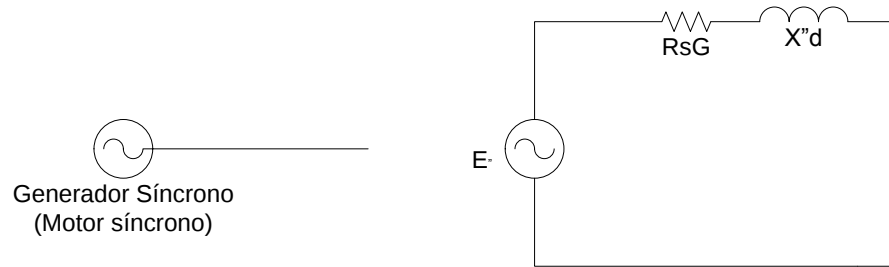


GENERADOR SINCRONO (MOTOR SINCRONO)




$$X''_d = x''_d \frac{U_N^2}{S}$$

U_N Tension Nominal

S_N Potencia nominal

X''_d Reactancia inicial

ALIMENTACION DE RED

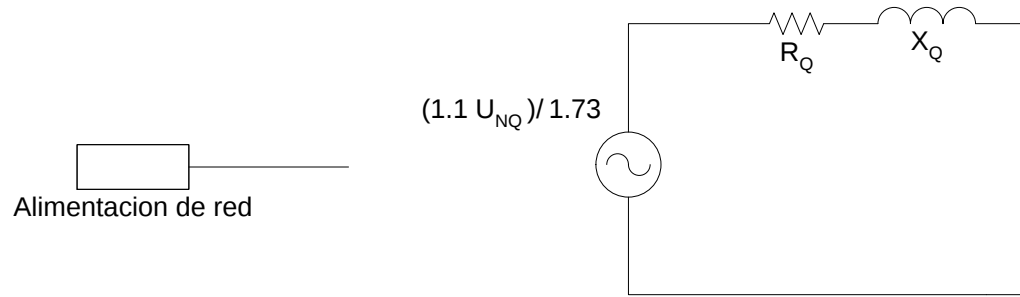


$$X_Q = 1.1 \frac{U_{NQ}^2}{S_{kQ}''}$$

U_{NQ} Tension No min al

S_{kQ} Potencia de corto circuito

TRANSFORMADOR

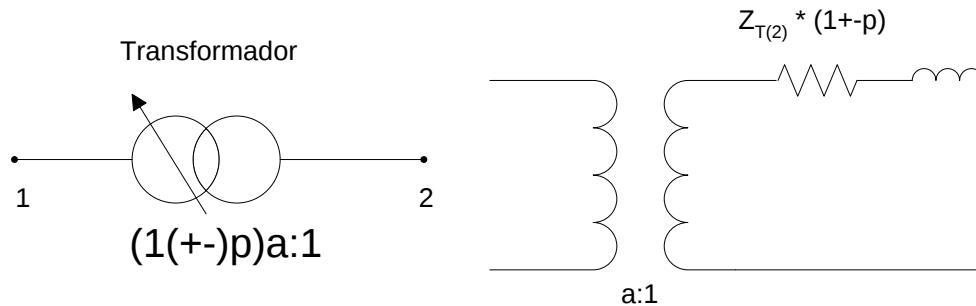

$$Z_{T(2)} = \frac{u_k \%}{100\%} * \frac{U_{n(2)}^2}{S_n}$$


$$X_{T(2)} = \sqrt{Z_{T(2)}^2 - R_{T(2)}^2}$$

S_n Potencia Nominal

u_k Tension de corto circuito %

a Relacion de transformacion en tap central

p Margen nominal de ajuste en p.u.

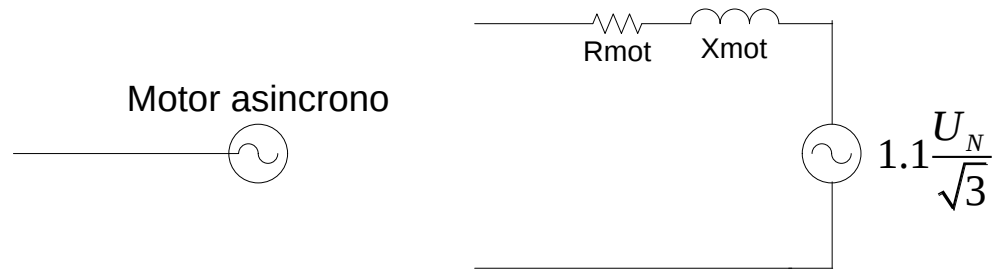

$$X_{Mot} = \frac{1}{I_{an}/I_{nMot}} * \frac{U_n}{\sqrt{3}I_{nMot}}$$

$$I_{nMot} = \frac{P_{Mot}}{(\sqrt{3}U_{nMot} \cos \varphi) \eta}$$

U_{nMot} Tension nominal del motor

I_{nMot} Corriente nominal del motor

I_{an}/I_{nMot} Corriente relativa de arranque

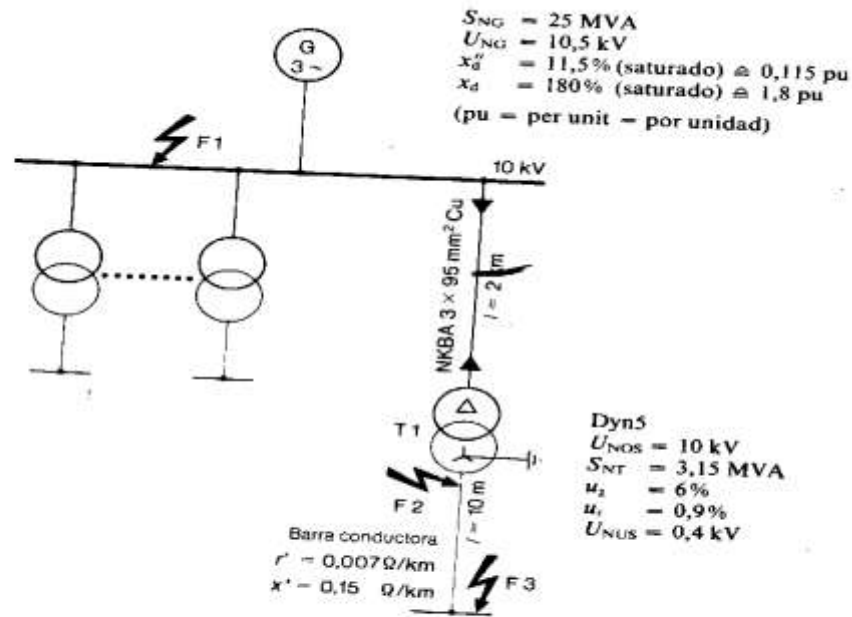


Fig. 1.3/6 Esquema de la red para el primer ejemplo de cálculo

Punto de defecto:

$$X_G = X_d = (x_d'' \cdot U_{NG}) / (100\% \cdot S_{NG}) = (11.5\% \cdot 10.52 \text{ kV}^2) / (100\% \cdot 25 \text{ MVA}) = 0.507 \text{ ohms}$$

$$R_G = 0.07 \cdot X_d = 0.07 \cdot 0.507 = 0.0355 \text{ ohms}$$

$$Z_G = R_G + jX_d = 0.0355 + j0.507 \text{ ohms}$$

$$Z_k = \sqrt{R_G^2 + X_d^2} = \sqrt{0.0355^2 + 0.507^2} = 0.508$$

Intensidad inicial de cortocircuito en corriente alterna:

$$I_k'' \text{ max 3 pol} = (c \cdot U_N) / (\sqrt{3} \cdot Z_k) = (1.1 \cdot 10 \text{ kV}) / (1.73 \cdot 0.508) = 12.52 \text{ KA}$$

$$I_s \text{ max 3 pol} = \kappa \cdot I_k'' \text{ max 3 pol} = 1.8 \cdot 1.41 \cdot 12.52 = 31.87 \text{ KA}$$